

HARDWARE DESCRIPTION LANGUAGE FOR DIGITAL DESIGN

數位設計硬體描述語言

Combinational and Sequential Logic Blocks

Materials partly adapted from “Digital System Designs and Practices Using Verilog HDL and FPGAs,” M.B. Lin.


OUTLINE

- Combinational Logic Blocks
- Sequential Logic Blocks


COMBINATIONAL LOGIC BLOCKS

DECODER BLOCK DIAGRAMS

- n -to- m decoders

 


(a) Noninverted output

 


(b) Inverted output

A 2-TO-4 DECODER EXAMPLE

 

E	x_1	x_0	Y_3	Y_2	Y_1	Y_0
1	ϕ	ϕ	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

(b) Function table

 

(c) Logic circuit

A 2-TO-4 DECODER EXAMPLE

// a 2-to-4 decoder with active low output

always @(x or enable_n)

if (enable_n) y = 4'b1111; else

case (x)


2'b00 : y = 4'b1110;

2'b01 : y = 4'b1101;

2'b10 : y = 4'b1011;

2'b11 : y = 4'b0111;

endcase

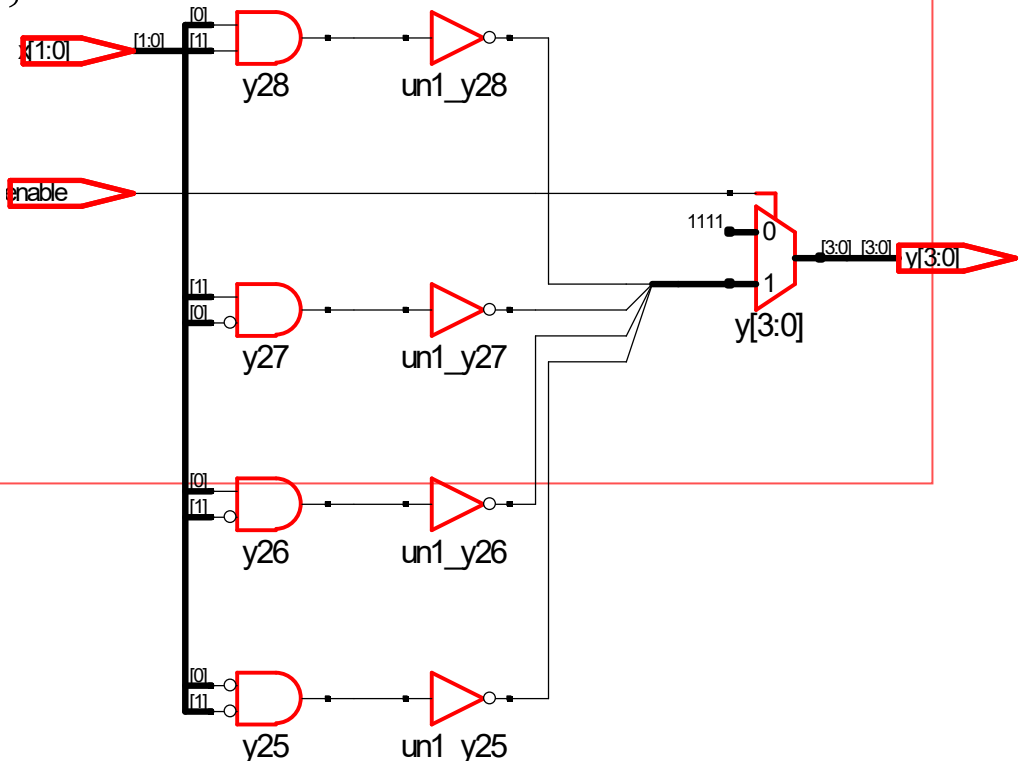

A 2-TO-4 DECODER WITH ENABLE CONTROL

// a 2-to-4 decoder with active-high output

always @(x or enable)

if (!enable) y = 4'b0000; else

case (x)


2'b00 : y = 4'b0001;

2'b01 : y = 4'b0010;

2'b10 : y = 4'b0100;


2'b11 : y = 4'b1000;

endcase

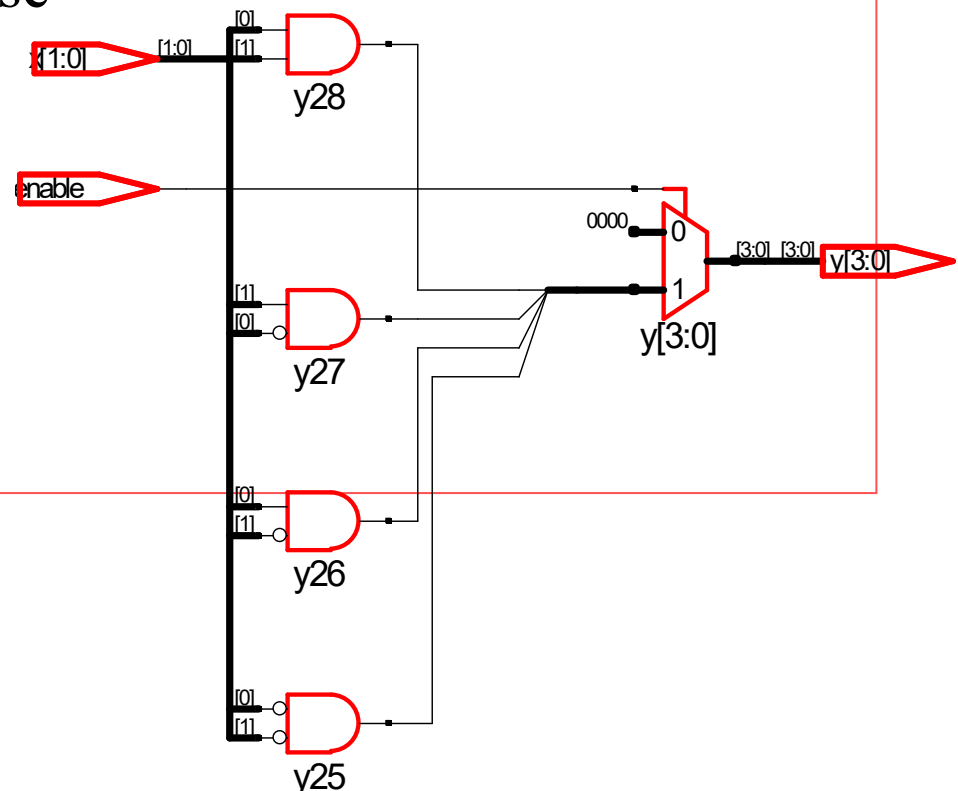


ENCODER BLOCK DIAGRAMS

- *m-to-n* encoders

 

(a) Noninverted output

 


(b) Inverted output

A 4-TO-2 ENCODER EXAMPLE

I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Function table

 

(b) Logic circuit

Q: What is the problem of this encoder?

A 4-TO-2 ENCODER EXAMPLE

// a 4-to-2 encoder using if ... else structure

always @(in) begin

if (in == 4'b0001) y = 0; else


if (in == 4'b0010) y = 1; else

if (in == 4'b0100) y = 2; else

if (in == 4'b1000) y = 3; else

y = 2'bx;

end

 

ANOTHER 4-TO-2 ENCODER EXAMPLE

// a 4-to-2 encoder using case structure

always @(in)

case (in)

4'b0001 : y = 0;


4'b0010 : y = 1;

4'b0100 : y = 2;


4'b1000 : y = 3;

default : y = 2'bx;

endcase

 

A 4-TO-2 PRIORITY ENCODER

 

(a) Block diagram

Input				Output	
I_3	I_2	I_1	I_0	A_1	A_0
0	0	0	1	0	0
0	0	1	ϕ	0	1
0	1	ϕ	ϕ	1	0
1	ϕ	ϕ	ϕ	1	1

(b) Function table

A 4-TO-2 PRIORITY ENCODER EXAMPLE

// using if ... else structure

assign valid_in = |in;

always @(in) begin

if (in[3]) y = 3; else


if (in[2]) y = 2; else

if (in[1]) y = 1; else

if (in[0]) y = 0; else

y = 2'bx;

end

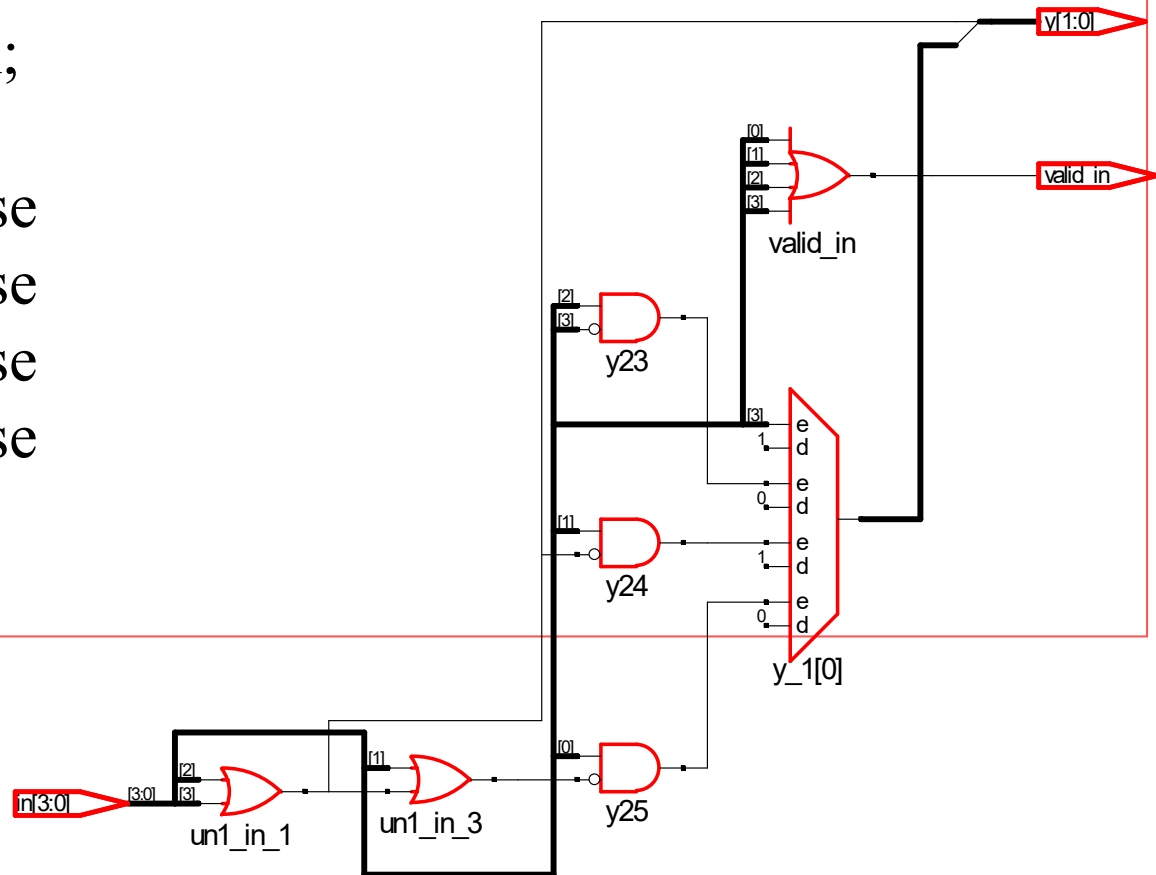

ANOTHER 4-TO-2 PRIORITY ENCODER EXAMPLE

// using casex structure

assign valid_in = |in;

always @(in) casex (in)

4'b1xxx: y = 3;


4'b01xx: y = 2;

4'b001x: y = 1;

4'b0001: y = 0;


default: y = 2'bx;

endcase

 


MULTIPLEXER BLOCK DIAGRAMS

- m -to-1 ($m = 2^n$) multiplexers

 


(a) Without enable control

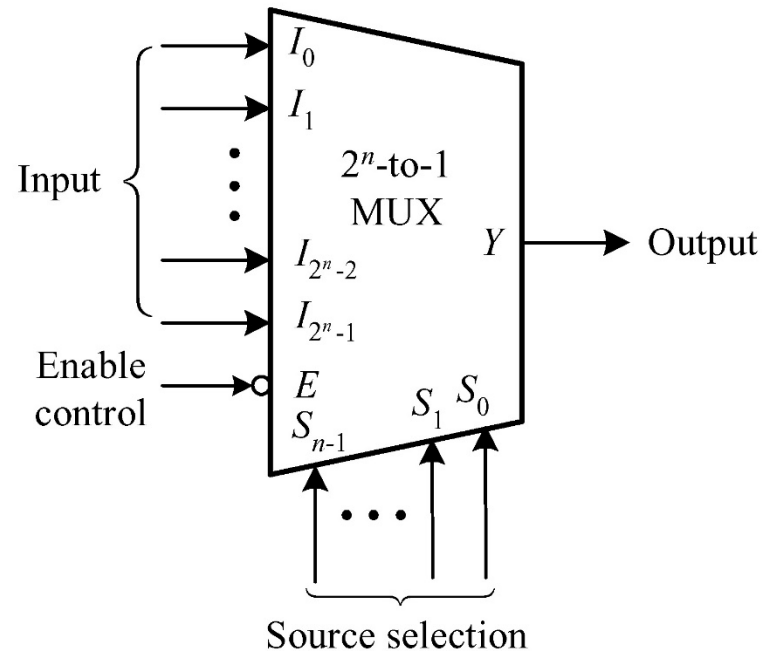

(b) With enable control

A 4-TO-1 MULTIPLEXER EXAMPLE


❖ Gate-based 4-to-1 multiplexers

 

(a) Logic symbol

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

 

(c) Logic circuit

AN N-BIT 4-TO-1 MULTIPLEXER EXAMPLE

// an N-bit 4-to-1 multiplexer using conditional operator

parameter N = 4; //

input [1:0] select;


input [N-1:0] in3, in2, in1, in0;

output [N-1:0] y;

assign y = select[1] ?

(select[0] ? in3 : in2) :

(select[0] ? in1 : in0);

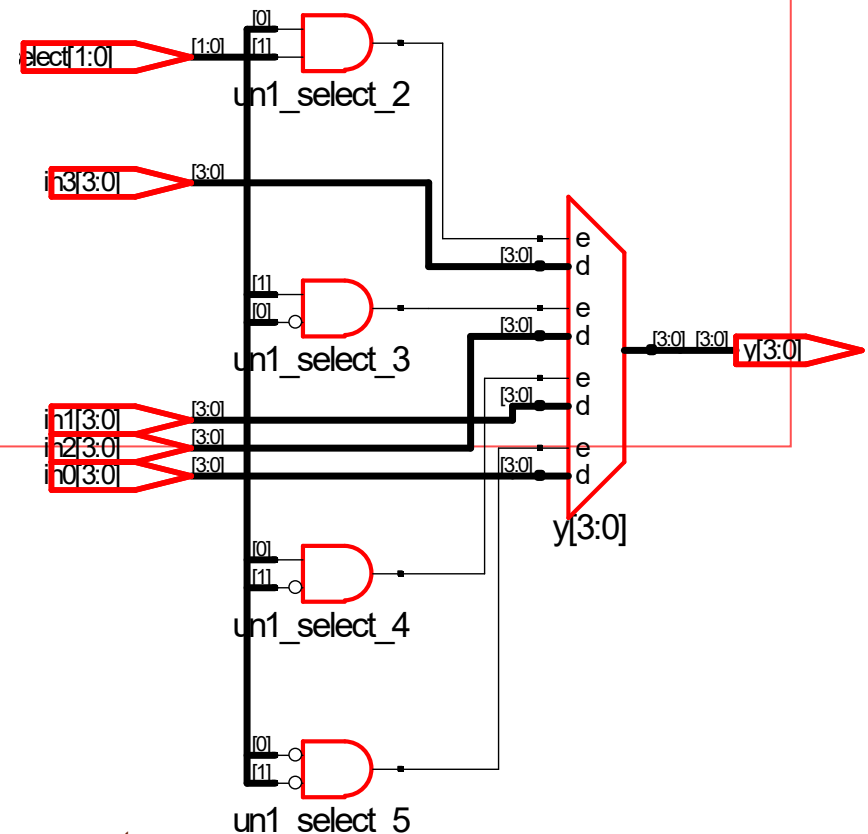

THE SECOND N-BIT 4-TO-1 MULTIPLEXER EXAMPLE

```
// an N-bit 4-to-1 multiplexer with enable control
```

```
parameter N = 4;
```

```
input [1:0] select;
```

```
input enable;
```

```
input [N-1:0] in3, in2, in1, in0;
```

```
output reg [N-1:0] y;
```

```
always @(select or enable or in0 or in1 or in2 or in3)
```

```
    if (!enable) y = {N{1'b0}};
```

```
    else y = select[1] ?
```


```
        (select[0] ? in3 : in2) :
```

```
        (select[0] ? in1 : in0) ;
```

THE THIRD N-BIT 4-TO-1 MULTIPLEXER EXAMPLE


// an N-bit 4-to-1 multiplexer using case structure
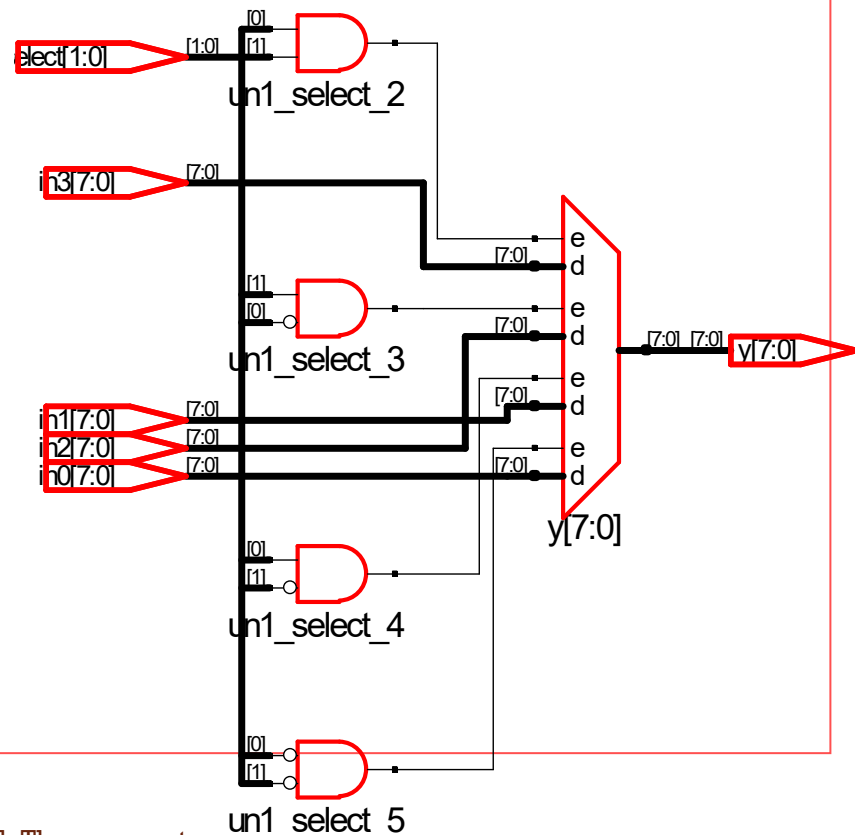
```
parameter N = 8;
input [1:0] select;
input [N-1:0] in3, in2, in1, in0;
output reg [N-1:0] y;
always @(*)
    case (select)
        2'b11: y = in3 ;
        2'b10: y = in2 ;
        2'b01: y = in1 ;
        2'b00: y = in0 ;
    endcase
```




DEMULTIPLEXER BLOCK DIAGRAMS

- 1-to- m ($m = 2^n$) demultiplexers

 


(a) Without enable control

 

(b) With enable control

A 1-TO-4 DEMULTIPLEXER EXAMPLE


❖ Gate-based 1-to-4 demultiplexers

 

(a) Logic symbol

E	S_1	S_0	Y_3	Y_2	Y_1	Y_0
1	ϕ	ϕ	0	0	0	0
0	0	0	0	0	0	D
0	0	1	0	0	D	0
0	1	0	0	D	0	0
0	1	1	D	0	0	0

(b) Function table

 

(c) Logic circuit

AN N-BIT 1-TO-4 DEMULTIPLEXER EXAMPLE

// an N-bit 1-to-4 demultiplexer using if ... else structure

parameter N = 4; // default width

input [1:0] select;

input [N-1:0] in;

output reg [N-1:0] y3, y2, y1, y0;

always @(select or in) begin


if (select == 3) y3 = in; else y3 = {N{1'b0}};

if (select == 2) y2 = in; else y2 = {N{1'b0}};

if (select == 1) y1 = in; else y1 = {N{1'b0}};

if (select == 0) y0 = in; else y0 = {N{1'b0}};

end

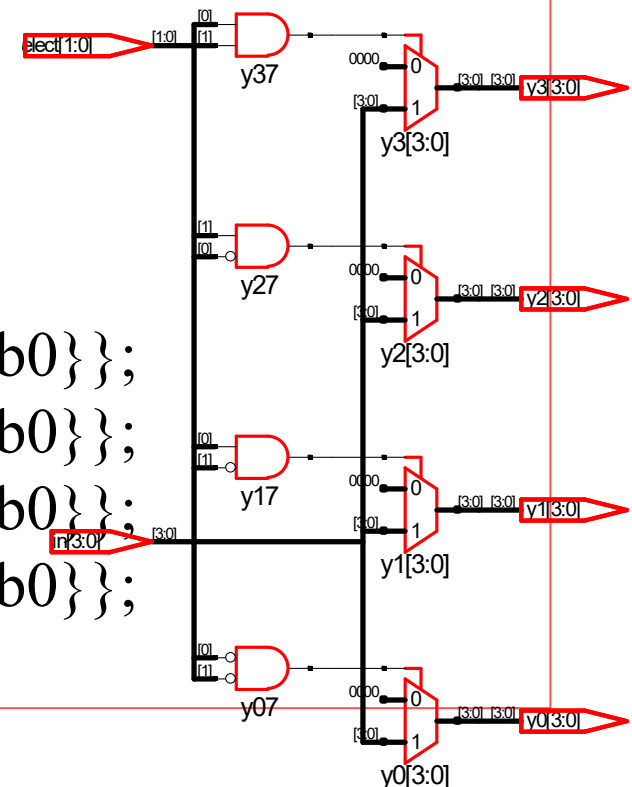


THE SECOND ~~N~~-BIT 1-TO-4 DEMULTIPLEXER EXAMPLE

```
// an N-bit 1-to-4 demultiplexer with enable control
parameter N = 4;    // Default width
...
output reg [N-1:0] y3, y2, y1, y0;
always @(select or in or enable) begin
    if (enable)begin
        if (select == 3) y3 = in; else y3 = {N{1'b0}};
        if (select == 2) y2 = in; else y2 = {N{1'b0}};
        if (select == 1) y1 = in; else y1 = {N{1'b0}};
        if (select == 0) y0 = in; else y0 = {N{1'b0}};
    end else begin
        y3 = {N{1'b0}}; y2 = {N{1'b0}}; y1 = {N{1'b0}}; y0 = {N{1'b0}}; end
    end
```

COMPARATORS


- A 4-bit comparator

 

A 4-bit cascadable comparator block diagram

COMPARATORS

- An 8-bit comparator

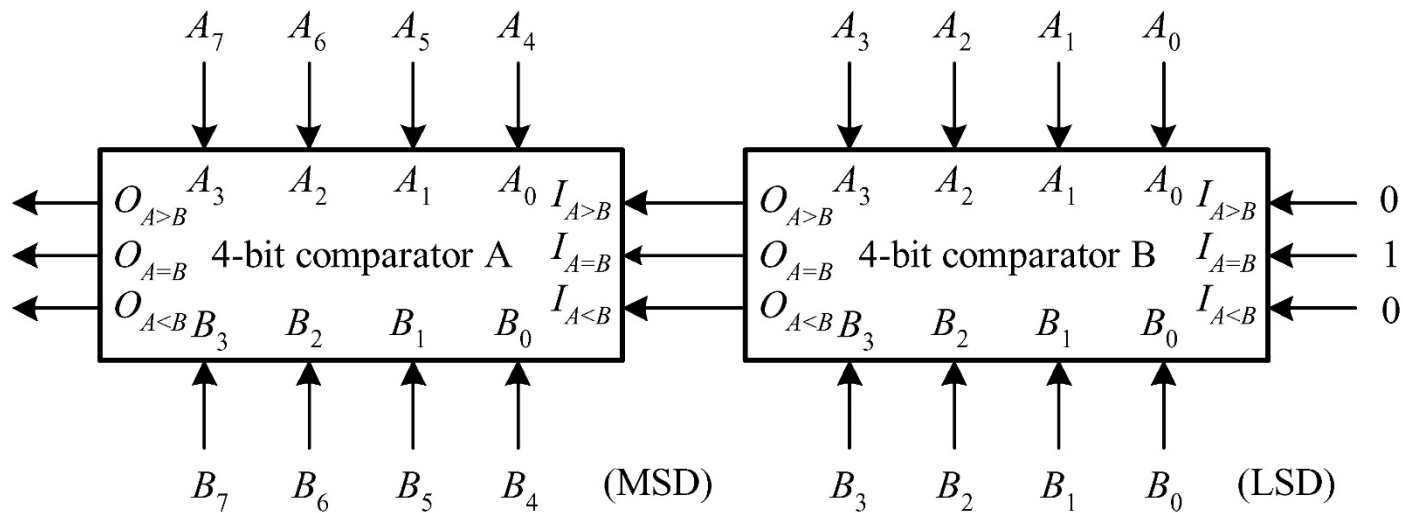

Q: What will happen if you set the input value (010) at the rightmost end to other values?

A SIMPLE COMPARATOR EXAMPLE

// an N-bit comparator module example

parameter N = 4; // default size


input [N-1:0] a, b;

output cgt, clt, ceq;

assign cgt = (a > b);

assign clt = (a < b);

assign ceq = (a == b);

 


A CASCADABLE COMPARATOR EXAMPLE

```

parameter N = 4;
// I/O port declarations
input    Iagtb, Iaeqb, Ialtb;
input    [N-1:0] a, b;
output   Oagtb, Oaeqb, Oaltb;
    
```

```

// dataflow modeling using relation operators
assign Oaeqb = (a == b) && (Iaeqb == 1); // =
assign Oagtb = (a > b) || ((a == b) && (Iagtb == 1)); // >
assign Oaltb = (a < b) || ((a == b) && (Ialtb == 1)); // <
    
```

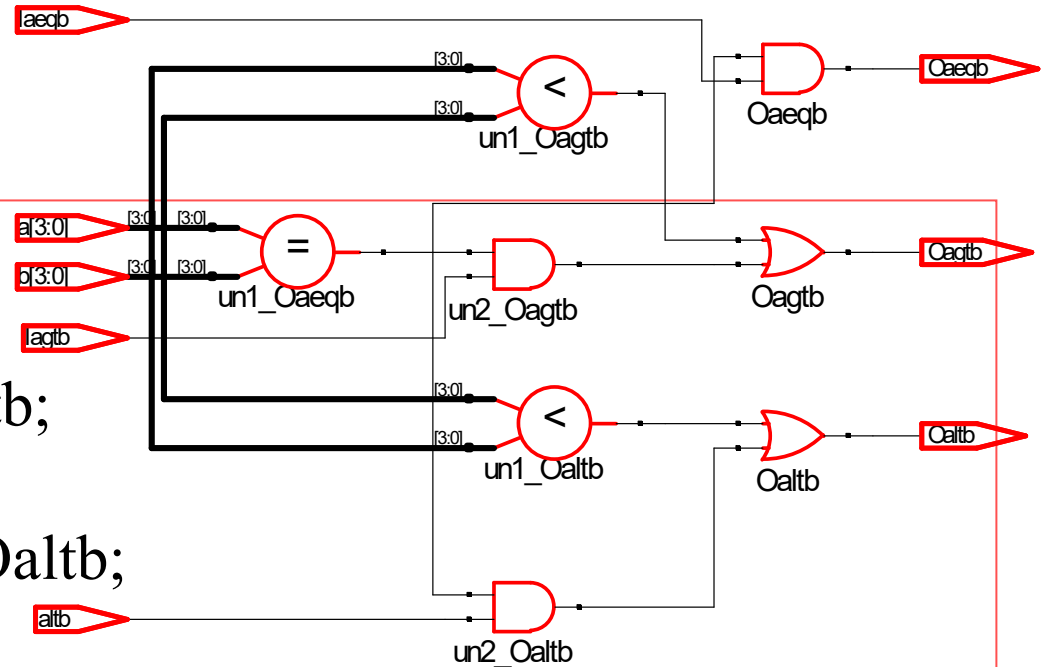

SEQUENTIAL LOGIC BLOCKS

ASYNCHRONOUS RESET D-TYPE FLIP-FLOPS

```
// asynchronous reset D-type flip-flop
module DFF_async_reset (clk, reset_n, d, q);
...
output reg q;

always @(posedge clk or negedge reset_n)
    if (!reset_n) q <= 0;
    else          q <= d;
```

Q: How would you model a *D*-type latch?

SYNCHRONOUS RESET D-TYPE FLIP-FLOPS


```
// synchronous reset D-type flip-flop
module DFF_sync_reset (clk, reset, d, q);
...
output reg q;

always @(posedge clk)
    if (reset) q <= 0;
    else      q <= d;
```

REGISTERS

- Registers (or data registers)
- A flip-flop
 - Area: 10 to 20x of an SRAM cell
- In Xilinx FPGAs
 - Flip-flops
 - Distributed memory
 - Block memory

DATA REGISTERS

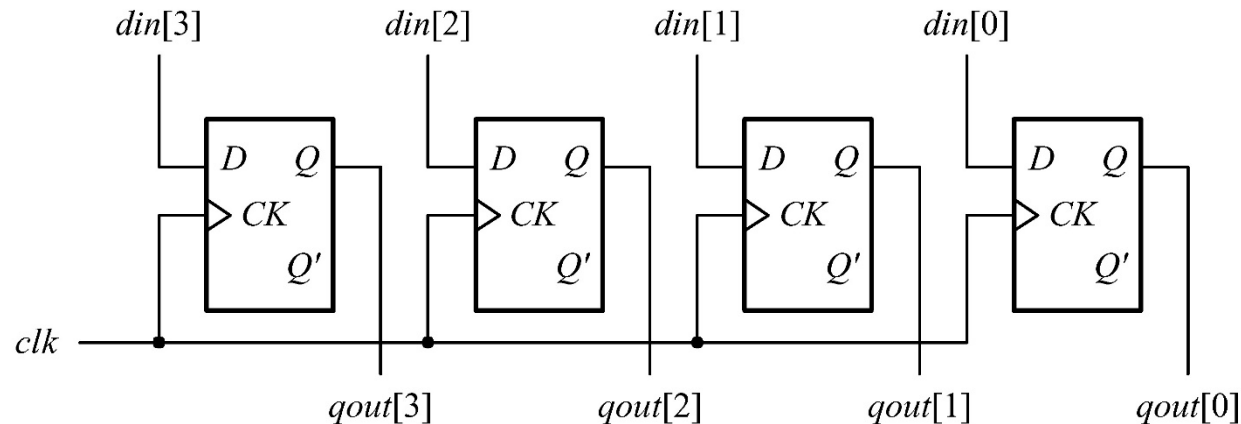

```
// an n-bit data register
module register(clk, din, qout);
parameter N = 4; // number of bits
...
input  [N-1:0] din;
output reg [N-1:0] qout;
always @(posedge clk) qout <= din;
```


DATA REGISTERS

```
// an n-bit data register with asynchronous reset
module register_reset (clk, reset_n, din, qout);
parameter N = 4; // number of bits
...
input  [N-1:0] din;
output reg [N-1:0] qout;
always @(posedge clk or negedge reset_n)
    if (!reset_n) qout <= {N{1'b0}};
    else          qout <= din;
```

DATA REGISTERS

```
// an N-bit data register with synchronous load and
// asynchronous reset
parameter N = 4; // number of bits
input  clk, load, reset_n;
input  [N-1:0] din;
output reg [N-1:0] qout;

always @(posedge clk or negedge reset_n)
    if (!reset_n)  qout <= {N{1'b0}};
    else if (load) qout <= din;
```

A REGISTER FILE

```
// an N-word register file with one-write and two-read ports
parameter M = 4; // number of address bits
parameter N = 16; // number of words, N = 2**M
parameter W = 8; // number of bits in a word
input  clk, wr_enable;
input  [W-1:0]  din;
output [W-1:0]  douta, doutb;
input  [M-1:0]  rd_addra, rd_addrb, wr_addr;
reg    [W-1:0]  reg_file [N-1:0];
...
assign douta = reg_file[rd_addra],
       doutb = reg_file[rd_addrb];
always @(posedge clk)
    if (wr_enable) reg_file[wr_addr] <= din;
```

Try to synthesize it and see what happens!!

AN SYNCHRONOUS RAM

// a synchronous RAM module example

parameter N = 16; // number of words

parameter A = 4; // number of address bits

parameter W = 4; // number of wordsize in bits

input [A-1:0] addr;

input [W-1:0] din;

input cs, wr, clk; // chip select, read-write control, and clock signals

output reg [W-1:0] dout;

reg [W-1:0] ram [N-1:0]; // declare an N * W memory array

always @(posedge clk)

if (cs) if (wr) ram[addr] <= din;


else dout <= ram[addr];

Try to synthesize it and see what happens!!


SHIFT REGISTERS

- Shift registers
- Parallel/serial format conversion
 - SISO (serial in serial out)
 - SIPO (serial in parallel out)
 - PISO (parallel in serial out)
 - PIPO (parallel in parallel out)

SHIFT REGISTERS

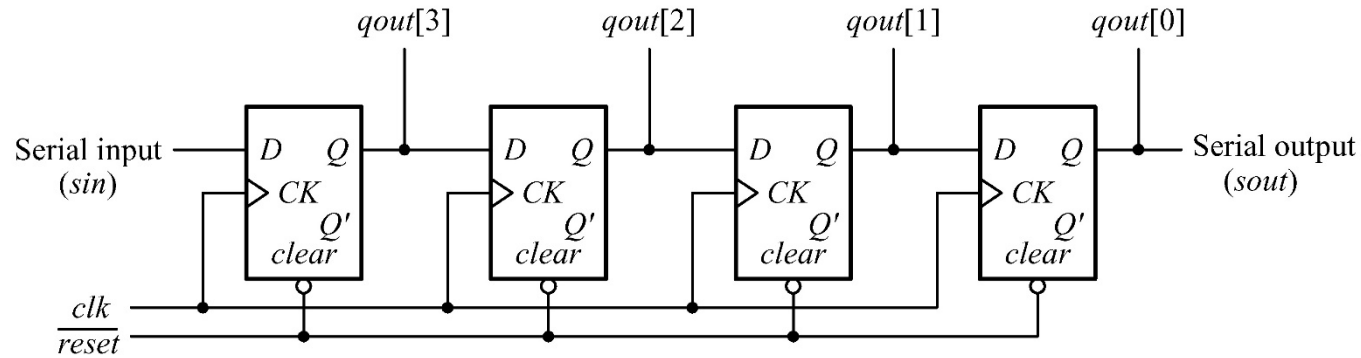

(a) Logic circuit

 

(b) Timing

SHIFT REGISTERS

```
// a shift register module example
module shift_register(clk, reset_n, din, qout);
Parameter N = 4; // number of bits
....
output reg [N-1:0] qout;

always @(posedge clk or negedge reset_n)
    if (!reset_n) qout <= {N{1'b0}};
    else          qout <= {din, qout[N-1:1]};
```

A SHIFT REGISTER WITH PARALLEL LOAD


```
// a shift register with parallel load module example
module shift_register_parallel_load
    (clk, load, reset_n, din, sin, qout);
    parameter N = 8; // number of bits
    ....
    input  [N-1:0] din;
    output reg [N-1:0] qout;

    always @(posedge clk or negedge reset_n)
        if (!reset_n) qout <= {N{1'b0}};
        else if (load) qout <= din;
        else          qout <= {sin, qout[N-1:1]};
```



UNIVERSAL SHIFT REGISTERS

- A universal shift register can carry out
 - SISO
 - SIPO
 - PISO
 - PIPO
- The register must have the following capabilities
 - Parallel load
 - Serial in and serial out
 - Shift left and shift right

UNIVERSAL SHIFT REGISTERS

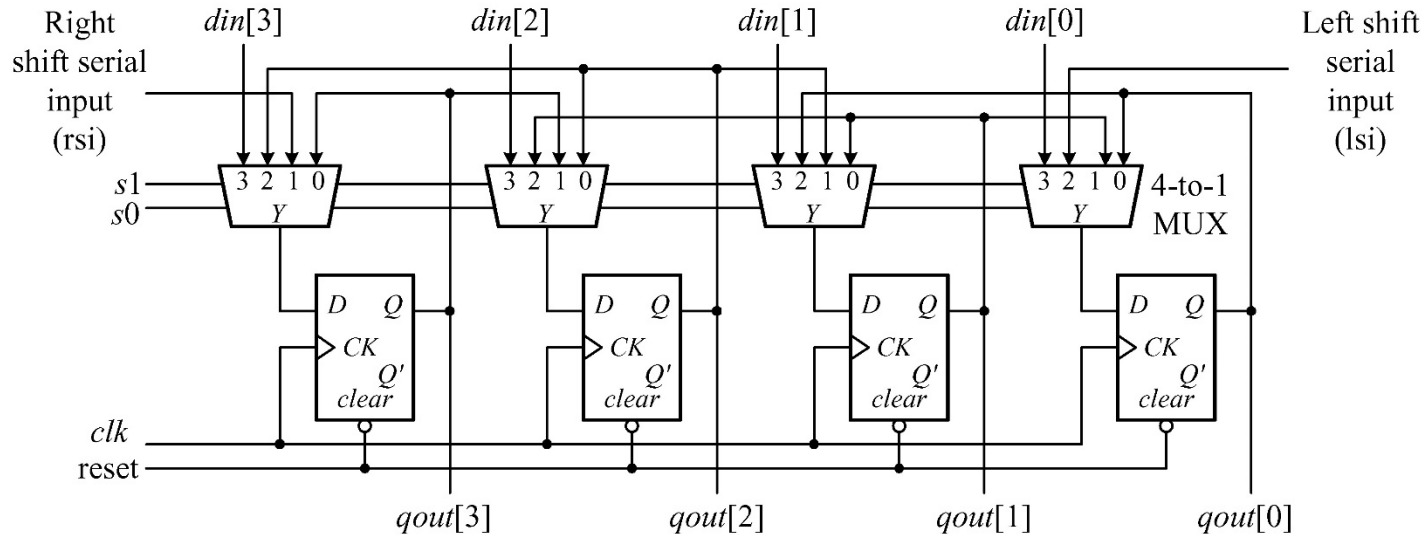 

(a) Logic diagram



(b) Logic symbol

s1	s0	Function
0	0	No change
0	1	Right shift
1	0	Left shift
1	1	Load data

(c) Function table

UNIVERSAL SHIFT REGISTERS

```
// a universal shift register module
module universal_shift_register (clk, reset_n, s1, s0, ...);
parameter N = 4; // define the default size
...
always @(posedge clk or negedge reset_n)
    if (!reset_n) qout <= {N{1'b0}};
    else case ({s1,s0})
        2'b00: ; // qout <= qout;           // No change
        2'b01: qout <= {lsi, qout[N-1:1]}; // Shift right
        2'b10: qout <= {qout[N-2:0], rsi}; // Shift left
        2'b11: qout <= din;                // Parallel load
    endcase
```


COUNTERS

- Counter
- Types
 - Counters
 - Timers


TYPES OF COUNTERS

- **Types of counters**
 - Asynchronous
 - Synchronous
- **Asynchronous (ripple) counters**
 - Binary counter (up/down counters)
- **Synchronous counters**
 - Binary counter (up/down counters)
 - BCD counter (up/down counters)
 - Gray counters (up/down counters)

BINARY RIPPLE COUNTERS

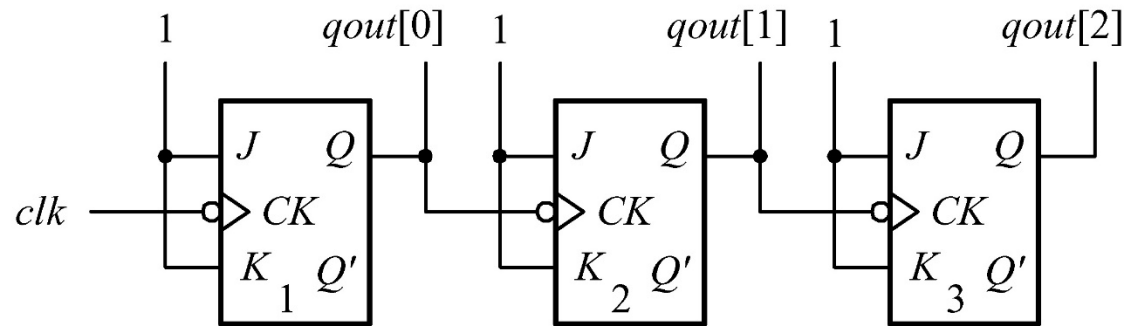

(a) Logic diagram

 

(b) Timing

BINARY RIPPLE COUNTERS

// a 3-bit ripple counter module example

```
module ripple_counter(clk, qout);
```

```
...
```

```
output reg [2:0] qout;
```

```
wire c0, c1;
```

// the body of the 3-bit ripple counter

```
assign c0 = qout[0], c1 = qout[1];
```

```
always @(negedge clk)
```

```
    qout[0] <= ~qout[0];
```

```
always @(negedge c0)
```

```
    qout[1] <= ~qout[1];
```

```
always @(negedge c1)
```

```
    qout[2] <= ~qout[2];
```

- Try to synthesize it and see what happens!!
- The output cannot be observed from simulators due to lacking initial values of qout.

BINARY RIPPLE COUNTERS

```
// a 3-bit ripple counter with enable control
module ripple_counter_enable(clk, enable, reset_n, qout);
...
output reg [2:0] qout;
wire c0, c1;
assign c0 = qout[0], c1 = qout[1];
always @(posedge clk or negedge reset_n)
    if (!reset_n) qout[0] <= 1'b0;
    else if (enable) qout[0] <= ~qout[0];
always @(posedge c0 or negedge reset_n)
    if (!reset_n) qout[1] <= 1'b0;
    else if (enable) qout[1] <= ~qout[1];
always @(posedge c1 or negedge reset_n)
    if (!reset_n) qout[2] <= 1'b0;
    else if (enable) qout[2] <= ~qout[2];
```


A BINARY RIPPLE COUNTER

```
// an N-bit ripple counter using generate blocks
parameter N = 4; // define the size of counter
...
output reg [N-1:0] qout;
genvar i;
generate for (i = 0; i < N; i = i + 1) begin: ripple_counter
    if (i == 0) // specify LSB
        always @(negedge clk or negedge reset_n)
            if (!reset_n) qout[0] <= 1'b0; else qout[0] <= ~qout[0];
    else // specify the rest bits
        always @(negedge qout[i-1] or negedge reset_n)
            if (!reset_n) qout[i] <= 1'b0; else qout[i] <= ~qout[i];
end endgenerate
```

A BINARY COUNTER EXAMPLE

```
module binary_counter(clk, enable, reset, qout, cout);  
parameter N = 4;  
...  
output reg [N-1:0] qout;  
output cout;    // carry output  
  
always @(posedge clk)  
    if (reset)      qout <= {N{1'b0}};  
    else if (enable) qout <= qout + 1;  
    // generate carry output  
assign #2 cout = &qout; // Why #2 is required ?
```

BINARY UP/DOWN COUNTERS --- VERSION 1

```
module binary_up_down_counter_reset
    (clk, enable, reset, upcnt, qout, cout, bout);
parameter N = 4;
...
output reg [N-1:0] qout;
output cout, bout; // carry and borrow outputs
always @(posedge clk)
    if (reset) qout <= {N{1'b0}};
    else if (enable) begin
        if (upcnt) qout <= qout + 1;
        else      qout <= qout - 1; end
assign #2 cout = &qout; // Why #2 is required ?
assign #2 bout = |qout;
```

BINARY UP/DOWN COUNTERS --- VERSION 2

```
module up_dn_bin_counter
    (clk, reset, eup, edn, qout, cout, bout);
    Parameter N = 4;
    ...
    output reg [N-1:0] qout;
    output cout, bout;

    always @(posedge clk)
        if (reset)    qout <= {N{1'b0}}; // synchronous reset
        else if (eup)  qout <= qout + 1;
        else if (edn)  qout <= qout - 1;
    assign #1 cout = (&qout)& eup; // generate carry out
    assign #1 bout = (~|qout)& edn; // generate borrow out
```

BINARY UP/DOWN COUNTERS --- VERSION 2

```
// the cascade of two up/down counters
module up_dn_bin_counter_cascaded(clk, reset,eup, ...);
parameter N = 4;
...
output [2*N-1:0] qout;
output cout, bout;
wire  cout1, bout1;


    up_dn_bin_counter #(4) up_dn_cnt1 (clk, reset,eup, edn, ...);
    up_dn_bin_counter #(4) up_dn_cnt2 (clk, reset, ...);
```

A MODULO R BINARY COUNTER

```
module modulo_r_counter(clk, enable, reset, qout, cout);  
parameter N = 4;  
parameter R= 10; // BCD counter  
...  
output reg [N-1:0] qout;  
...  
assign cout = (qout == R - 1);  
always @(posedge clk)  
    if (reset) qout <= {N{1'b0}};  
    else begin  
        if (enable) if (cout) qout <= 0;  
        else      qout <= qout + 1; end
```

SEQUENCE GENERATORS

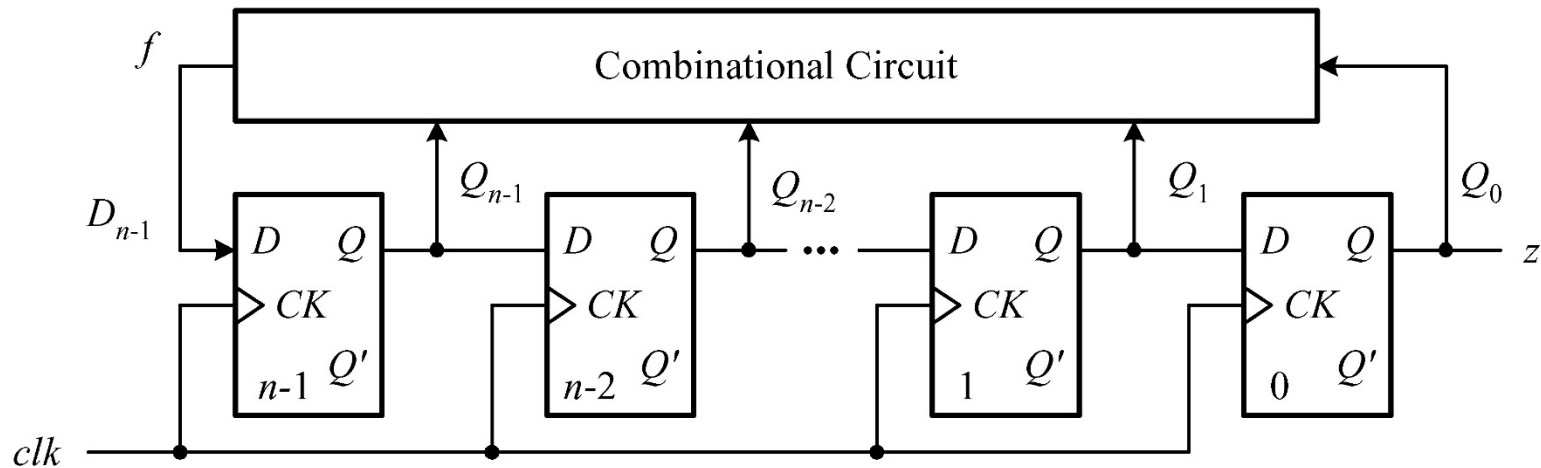- We only focus on the following three circuits
 - PR (pseudo random)-sequence generator
 - Ring counter
 - Johnson counter




PRIMITIVE POLYNOMIALS


n	$f(x)$	n	$f(x)$	n	$f(x)$
1, 2, 3, 4, 6, 7, 15, 22, 60	$1+x+x^n$	24	$1+x+x^2+x^7+x^n$	43	$1+x+x^5+x^6+x^n$
		26	$1+x+x^2+x^6+x^n$	44, 50	$1+x+x^{26}+x^{27}+x^n$
5, 11, 21, 29	$1+x^2+x^n$	30	$1+x+x^2+x^{23}+x^n$	45	$1+x+x^3+x^4+x^n$
10, 17, 20, 25, 28, 31, 41, 52	$1+x^3+x^n$	32	$1+x+x^2+x^{22}+x^n$	46	$1+x+x^{20}+x^{21}+x^n$
		33	$1+x^{13}+x^n$	48	$1+x+x^{27}+x^{28}+x^n$
9	$1+x^4+x^n$	34	$1+x+x^{14}+x^{15}+x^n$	49	$1+x^9+x^n$
23, 47	$1+x^5+x^n$	35	$1+x^2+x^n$	51, 53	$1+x+x^{15}+x^{16}+x^n$
18	$1+x^7+x^n$	36	$1+x^{11}+x^n$	54	$1+x+x^{36}+x^{37}+x^n$
8	$1+x^2+x^3+x^4+x^n$	37	$1+x^2+x^{10}+x^{12}+x^n$	55	$1+x^{24}+x^n$
12	$1+x+x^4+x^6+x^n$	38	$1+x+x^5+x^6+x^n$	56, 59	$1+x+x^{21}+x^{22}+x^n$
13	$1+x+x^3+x^4+x^n$	39	$1+x^4+x^n$	57	$1+x^7+x^n$
14, 16	$1+x^3+x^4+x^5+x^n$	40	$1+x^2+x^{19}+x^{21}+x^n$	58	$1+x^{19}+x^n$
19, 27	$1+x+x^2+x^5+x^n$	42	$1+x+x^{22}+x^{23}+x^n$		

$$f(x) = \sum_{i=0}^n a_i x^i = a_0 + a_1 x + a_2 x^2 + \dots + a_n x^n$$

MAXIMAL LENGTH SEQUENCE GENERATORS

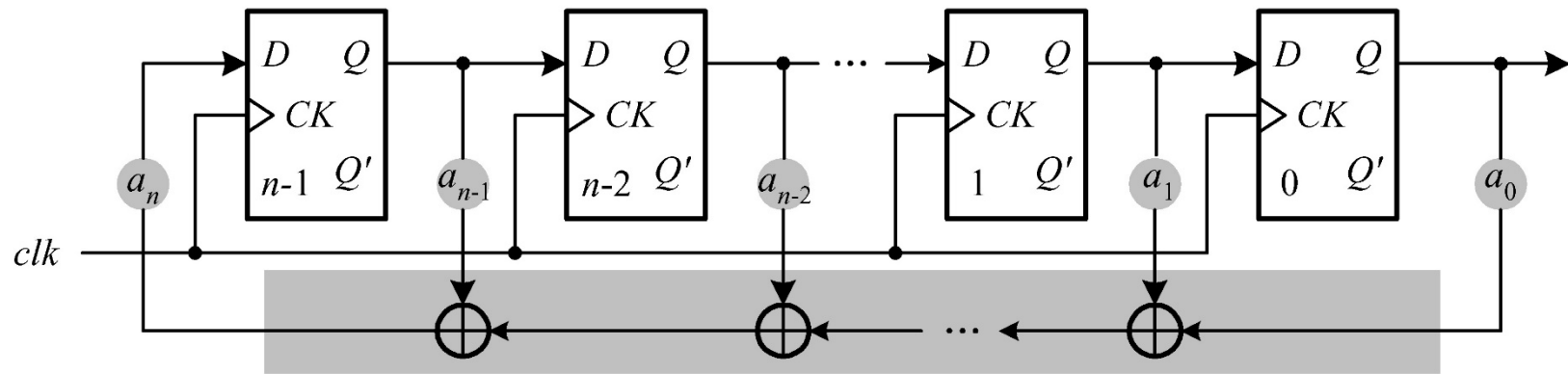


(a) Standard format

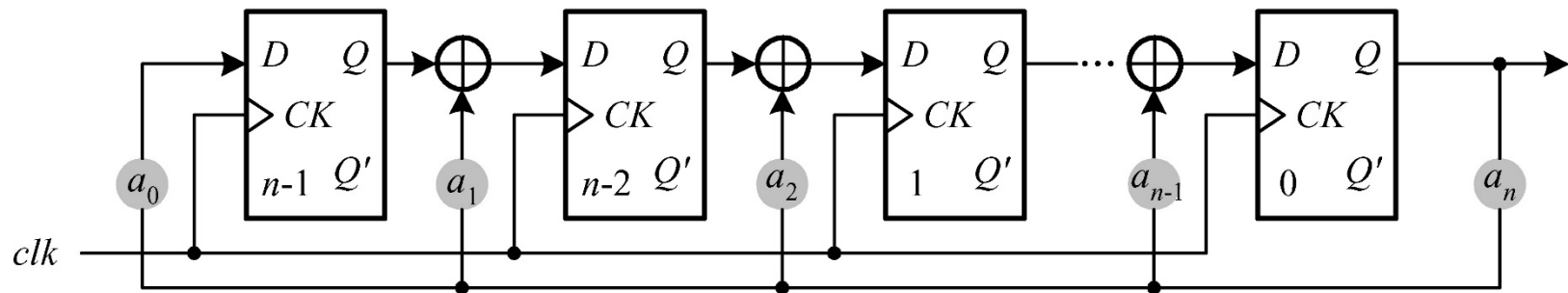

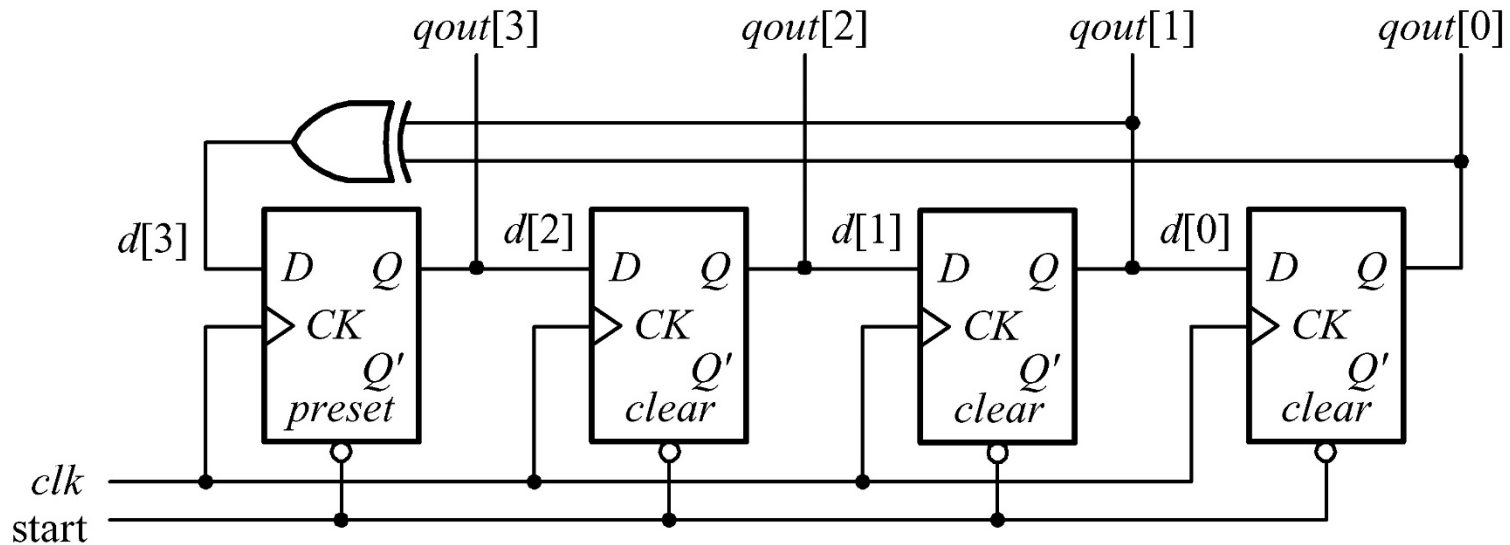(b) Modular format

A PR-SEQUENCE GENERATOR EXAMPLE

- A 4-bit example
 - primitive polynomial: $1 + x + x^4$



A PR-SEQUENCE GENERATOR EXAMPLE


```
// an N-bit pr_sequence generator module --- in standard form
module pr_sequence_generate (clk, qout);
parameter N = 4; // define the default size
parameter [N:0] tap = 5'b10011;
...
output reg [N-1:0] qout = 4'b0100;
wire d;
...
assign d = ^(tap[N-1:0] & qout[N-1:0]);
always @(posedge clk)
    qout <= {d, qout[N-1:1]};
```

Q: Write an N-bit pr_sequence generator in modular form.

A PR-SEQUENCE GENERATOR EXAMPLE


```
// an N-bit pr_sequence generator module --- in standard form
module pr_sequence_generate (clk, start, qout);
parameter N = 4; // define the default size
parameter [N:0] tap = 5'b10011;
...
output reg [N-1:0] qout;
wire d;
...
assign d = ^(tap[N-1:0] & qout[N-1:0]);
always @(posedge clk or posedge start)
    if (start) qout <= {1'b1, {N-1{1'b0}}};
    else      qout <= {d, qout[N-1:1]};
```

RING COUNTERS

 

```
// a ring counter with initial value
module ring_counter(clk, start, qout);
parameter N = 4;
...
output reg [0:N-1] qout;
...
always @(posedge clk or posedge start)
    if (start) qout <= {1'b1, {N-1 {1'b0}}};
    else      qout <= {qout[N-1], qout[0:N-2]};
```

JOHNSON COUNTERS

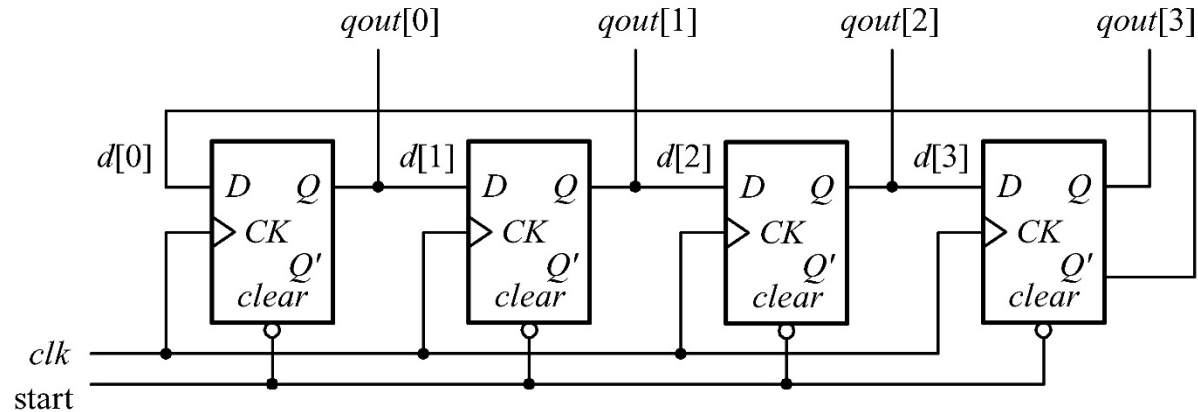


```
// Johnson counter with initial value
module ring_counter(clk, start, qout);
parameter N = 4; // define the default size
...
output reg [0:N-1] qout;
...
always @(posedge clk or posedge start)
    if (start) qout <= {N{1'b0}};
    else      qout <= {~qout[N-1], qout[0:N-2]};
```

TIMING GENERATORS

- A timing generator
- Multiphase clock signals
 - Ring counter
 - Binary counter with decoder
- Digital monostable circuits
 - Retriggerable
 - Nonretriggerable


MULTIPHASE CLOCK SIGNALS

 - Ways of generation
 - Ring counter approach
 - Binary counter with decoder approach



MULTIPHASE CLOCK GENERATORS

- Binary counter with decoder approach

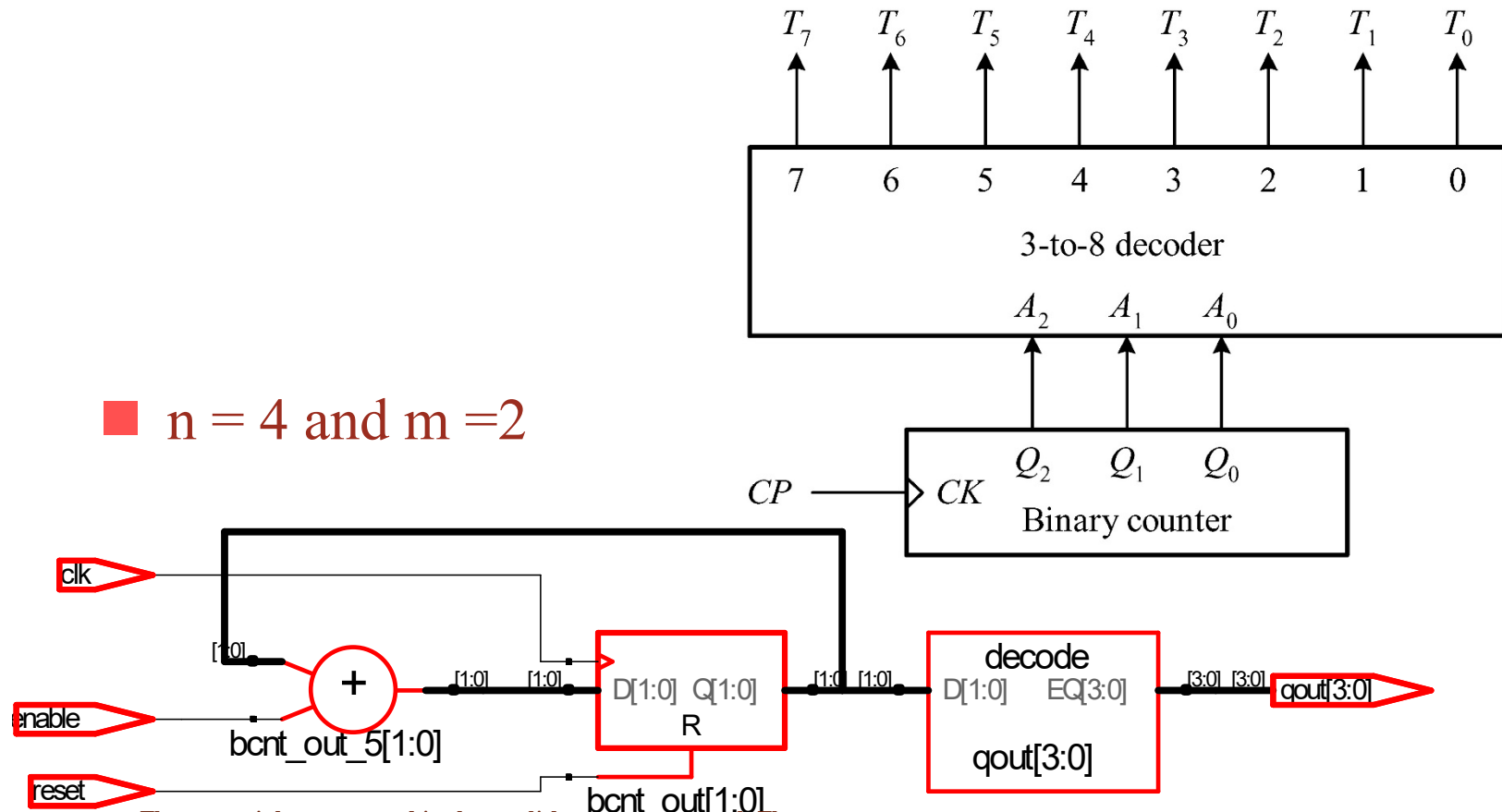

MULTIPHASE CLOCK GENERATORS

```
// a binary counter with decoder serve as a timing generator
module binary_counter_timing_generator(clk, reset, enable, qout);
parameter N = 8; // the number of phases
parameter M = 3; // the bit number of binary counter
...
output reg [N-1:0] qout;
reg [M-1:0] bcnt_out;
...
always @(posedge clk or posedge reset)
    if (reset) bcnt_out <= {M{1'b0}};
    else if (enable) bcnt_out <= bcnt_out + 1;
...
always @(bcnt_out)
    qout = {N-1{1'b0}, 1'b1} << bcnt_out;
```