

# HARDWARE DESCRIPTION LANGUAGE FOR DIGITAL DESIGN

數位設計硬體描述語言

## Hierarchical Structure Modeling

Materials partly adapted from “Digital System Designs and Practices Using Verilog HDL and FPGAs,” M.B. Lin.

# OUTLINE

- Verilog Basics
- Structural Modeling
- Dataflow Modeling
- Behavioral Modeling
- Tasks and Functions
- **Hierarchical Structure Modeling**

# HIERARCHICAL STRUCTURE MODELING

# MODULE DEFINITIONS

// port list style

```
module module_name [#(parameter_declarations)][port_list];  
parameter_declarations; // if no parameter ports are used  
port_declarations;  
other_declaration;  
statements;  
endmodule
```

// port list declaration style

```
module module_name [#(parameter_declarations)][port_declarations];  
parameter_declarations; // if no parameter ports are used  
other_declarations;  
statements;  
endmodule
```

# PORT DECLARATIONS

- Three types

- input

- output

- inout



```
module adder(x, y, c_in, sum, c_out);  
input [3:0] x, y;  
input c_in;  
output reg [3:0] sum;  
output reg c_out;
```

# TYPES OF PARAMETERS

- module parameters
  - parameter
  - localparam
- specify parameters

```
parameter SIZE = 7;  
parameter WIDTH_BUSA = 24, WIDTH_BUSB = 8;  
parameter signed [3:0] mux_selector = 4'b0;
```

# CONSTANTS SPECIFIED OPTIONS

- ``define` compiler directive

``define BUS_WIDTH 8`

- Parameter

`parameter BUS_WIDTH = 8;`

- `localparam`

`localparam BUS_WIDTH = 8;`

# PARAMETER PORTS

```
module module_name
#(parameter SIZE = 7,
  parameter WIDTH_BUSA = 24, WIDTH_BUSB = 8,
  parameter signed [3:0] mux_selector = 4'b0
)
(port list or port list declarations)
...
endmodule
```



# MODULE INSTANTIATION

- **Syntax**

```
module_name [#(parameters)]
            instance_name [range]([ports]);
module_name [#(parameters)]
            instance_name
            [{,instance_name}]([ports]);
```

# PORT CONNECTION RULES

- Named association

`.port_id1(port_expr1), ..., .port_idn(port_exprn)`

- Positional association

`port_expr1, ..., port_exprn`

# PARAMETERIZED MODULES

- An example

```
module adder_nbit(x, y, c_in, sum, c_out);  
parameter N = 4; // set default value  
input [N-1:0] x, y;  
input c_in;  
output [N-1:0] sum;  
output c_out;  
  
assign {c_out, sum} = x + y + c_in;  
endmodule
```

# MODULE PARAMETERS VALUES

- Ways to change module parameters values
  - defparam statement
  - module instance parameter value assignment

# OVERRIDING PARAMETERS

- Using the defparam statement

```
module counter_nbits (clock, clear, qout);  
    parameter N = 4; // define counter size  
    ...  
    always @(negedge clock or posedge clear)  
    begin        // qout <= (qout + 1) % 2^n  
        if (clear) qout <= {N{1'b0}};  
        else      qout <= (qout + 1);  
    End
```

```
// define top level module
```

```
...  
output [3:0] qout4b;  
output [7:0] qout8b;  
// instantiate two counter modules  
defparam cnt_4b.N = 4, cnt_8b.N = 8;  
counter_nbits cnt_4b (clock, clear, qout4b);  
counter_nbits cnt_8b (clock, clear, qout8b);
```

# OVERRIDING PARAMETERS

- Using module instance  
parameter value  
assignment---  
one parameter

```
module counter_nbits (clock, clear, qout);  
parameter N = 4; // define counter size  
...  
always @(negedge clock or posedge clear)  
begin          // qout <= (qout + 1) % 2^n;  
    if (clear) qout <= {N{1'b0}};  
    else      qout <= (qout + 1);  
end
```

```
// define top level module  
...  
output [3:0] qout4b;  
output [7:0] qout8b;  
// instantiate two counter modules  
counter_nbits #(4) cnt_4b (clock, clear, qout4b);  
counter_nbits #(8) cnt_8b (clock, clear, qout8b);
```

# OVERRIDING PARAMETERS


- Using module instance  
parameter value  
assignment  
--- two parameters

```
// define top level module  
module ...  
...  
hazard_static #(4, 8) example (x, y, z, f);
```

```
module hazard_static (x, y, z, f);  
parameter delay1 = 2, delay2 = 5;  
...  
and #delay2 a1 (b, x, y);  
not #delay1 n1 (a, x);  
and #delay2 a2 (c, a, z);  
or #delay2 o2 (f, b, c);  
endmodule
```

```
hazard_static #(.delay2(4), .delay1(6))  
example (x, y, z, f);
```

 - parameter value assignment by name ---  
minimize the chance of error!



# HIERARCHICAL PATH NAMES

- An identifier can be defined within
  - Modules
  - Tasks
  - Functions
  - Named blocks (See Section 7.1.3)
- Hierarchical path names

```
4bit_adder          // top level --- 4bit_adder
4bit_adder.fa_1     // fa_1 within 4bit_adder
4bit_adder.fa_1.ha_1 // ha_1 within fa_1
4bit_adder.fa_1.ha_1.xor1 // xor1 within ha_1
4bit_adder.fa_1.ha_1.xor1.S // net s within xor1
```



# GENERATE BLOCK STRUCTURES

- The keywords used
  - **generate** and **endgenerate**

```
// convert Gray code into binary code
parameter SIZE = 8;
input [SIZE-1:0] gray;
output [SIZE-1:0] bin;
genvar i;
generate for (i = 0; i < SIZE; i = i + 1) begin: bit
    assign bin[i] = ^gray[SIZE-1:i];
end endgenerate
```

# THE GENERATE LOOP CONSTRUCT

```
// convert Gray code into binary code
parameter SIZE = 8;
input [SIZE-1:0] gray;
output [SIZE-1:0] bin;
reg [SIZE-1:0] bin;

genvar i;
generate for (i = 0; i < SIZE; i = i + 1) begin:bit
    always @(*)
        bin[i] = ^gray[SIZE - 1: i];
end endgenerate
```

# AN N-BIT ADDER

```
// define a full adder at dataflow level.  
module full_adder(x, y, c_in, sum, c_out);  
// I/O port declarations  
input  x, y, c_in;  
output sum, c_out;  
// Specify the function of a full adder.  
    assign {c_out, sum} = x + y + c_in;  
endmodule
```

# AN N-BIT ADDER

```
module adder_nbit(x, y, c_in, sum, c_out);  
...  
genvar i;  
wire [N-2:0] c;    // internal carries declared as nets.  
generate for (i = 0; i < N; i = i + 1) begin: adder  
    if (i == 0)      // specify LSB  
        full_adder fa (x[i], y[i], c_in, sum[i], c[i]);  
    else if (i == N-1) // specify MSB  
        full_adder fa (x[i], y[i], c[i-1], sum[i], c_out);  
    else              // specify other bits  
        full_adder fa (x[i], y[i], c[i-1], sum[i], c[i]);  
end endgenerate
```

# AN N-BIT ADDER

```
module adder_nbit(x, y, c_in, sum, c_out);  
...  
genvar i;  
wire [N-2:0] c;    // internal carries declared as nets.  
generate for (i = 0; i < N; i = i + 1) begin: adder  
    if (i == 0)      // specify LSB  
        assign {c[i], sum[i]} = x[i] + y[i] + c_in;  
    else if (i == N-1) // specify MSB  
        assign {c_out, sum[i]} = x[i] + y[i] + c[i-1];  
    else              // specify other bits  
        assign {c[i], sum[i]} = x[i] + y[i] + c[i-1];  
end endgenerate
```

# AN N-BIT ADDER

```
module adder_nbit(x, y, c_in, sum, c_out);  
...  
genvar i;  
reg [N-2:0] c;    // internal carries declared as nets.  
generate for (i = 0; i < N; i = i + 1) begin: adder  
    if (i == 0)    // specify LSB  
        always @(*) {c[i], sum[i]} = x[i] + y[i] + c_in;  
    else if (i == N-1) // specify MSB  
        always @(*) {c_out, sum[i]} = x[i] + y[i] + c[i-1];  
    else           // specify other bits  
        always @(*) {c[i], sum[i]} = x[i] + y[i] + c[i-1];  
end endgenerate
```

# A TWO'S COMPLEMENT ADDER

```
module twos_adder_nbit(x, y, mode, sum, c_out);  
...  
genvar i;  
wire [N-2:0] c; // internal carries declared as nets.  
wire [N-1:0] t; // true/ones complement outputs  
generate for (i = 0; i < N; i = i + 1) begin:  
// ones_complement_generator  
    xor xor_ones_complement (t[i], y[i], mode);  
end endgenerate
```


# A TWO'S COMPLEMENT ADDER

```
generate for (i = 0; i < N; i = i + 1) begin: adder
  if (i == 0)           // specify LSB
    full_adder fa (x[i], t[i], mode, sum[i], c[i]);
  else if (i == N-1) // specify MSB
    full_adder fa (x[i], t[i], c[i-1], sum[i], c_out);
  else                 // specify other bits
    full_adder fa (x[i], t[i], c[i-1], sum[i], c[i]);
end endgenerate
```



# A TWO'S COMPLEMENT ADDER


- The RTL schematic from Synplify Pro.

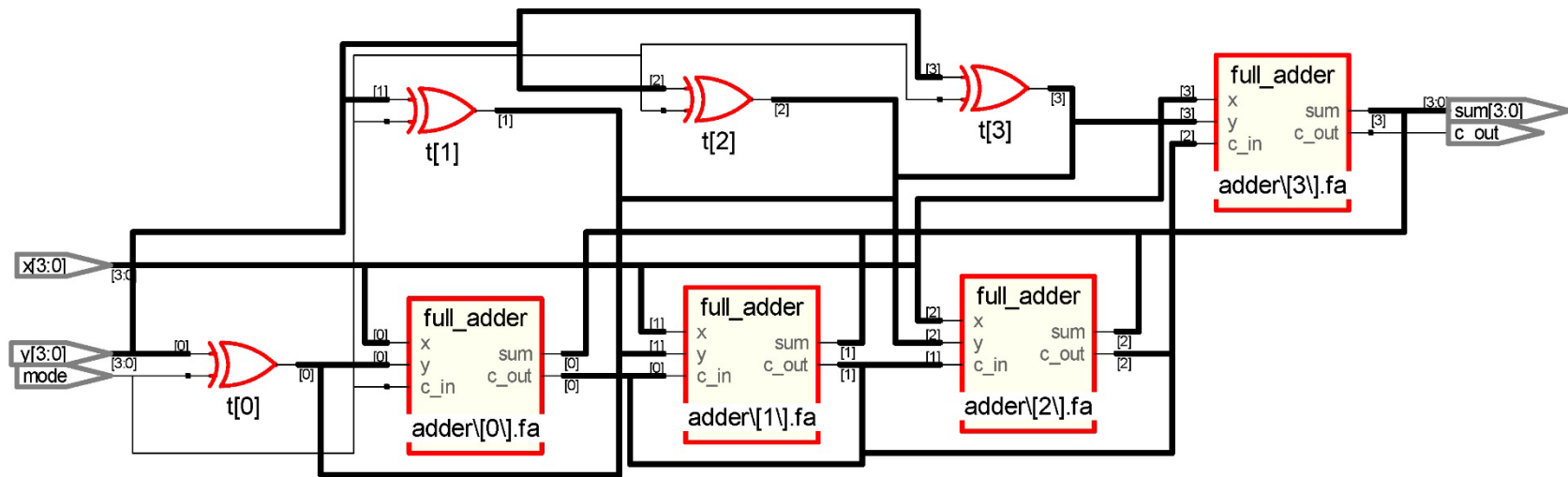

(a) The RTL schematic
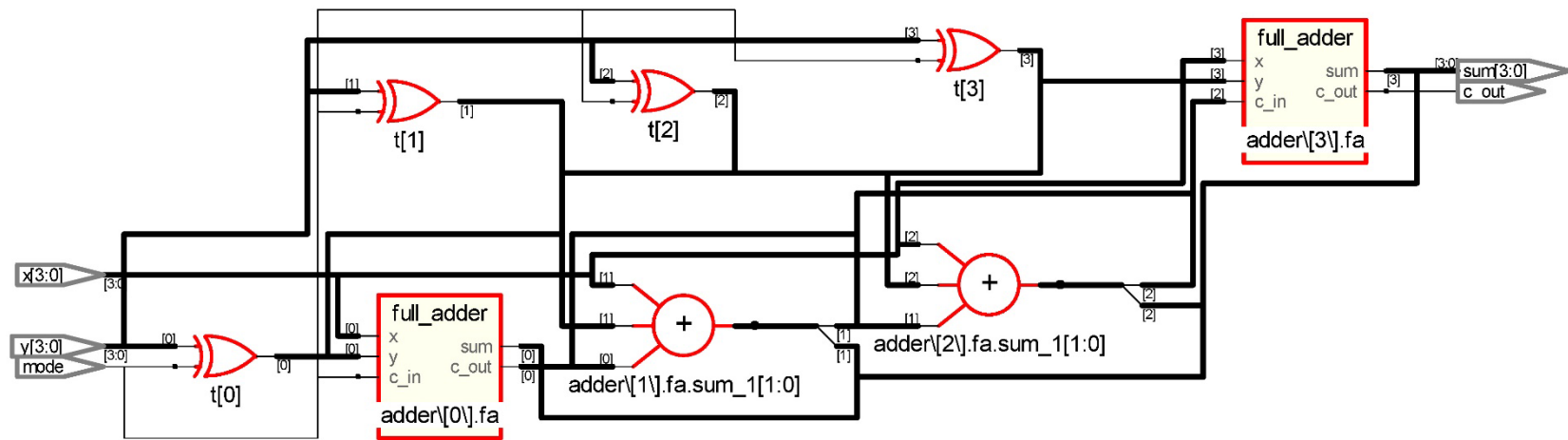
# A TWO'S COMPLEMENT ADDER

- After dissolving the second and the third bits



(b) After dissolving the second and the third full adder modules

# THE GENERATE CASE CONSTRUCT

```
generate for (i = 0; i < N; i = i + 1) begin: adder
  case (i)
    0: assign {c[i], sum[i]} = x[i] + y[i] + c_in;
    N-1: assign {c_out, sum[i]} = x[i] + y[i] + c[i-1];
    default: assign {c[i], sum[i]} = x[i] + y[i] + c[i-1];
  endcase
end endgenerate
```